

**DO NOT OPEN THIS TEST BOOKLET UNTIL YOU ARE ASKED TO DO SO**

T.B.C. : B-FRF-M-DSA

Test Booklet Series

Serial No.

**TEST BOOKLET**  
**ELECTRONICS AND**  
**TELECOMMUNICATION**  
**ENGINEERING**

**A**

**Paper I**

Time Allowed : Two Hours

Maximum Marks : 200

**INSTRUCTIONS**

1. IMMEDIATELY AFTER THE COMMENCEMENT OF THE EXAMINATION, YOU SHOULD CHECK THAT THIS TEST BOOKLET **DOES NOT** HAVE ANY UNPRINTED OR TORN OR MISSING PAGES OR ITEMS, ETC. IF SO, GET IT REPLACED BY A COMPLETE TEST BOOKLET.
2. PLEASE NOTE THAT IT IS THE CANDIDATE'S RESPONSIBILITY TO ENCODE AND FILL IN THE ROLL NUMBER AND TEST BOOKLET SERIES CODE A, B, C OR D CAREFULLY AND WITHOUT ANY OMISSION OR DISCREPANCY AT THE APPROPRIATE PLACES IN THE *OMR* ANSWER SHEET. ANY OMISSION/DISCREPANCY WILL RENDER THE ANSWER SHEET LIABLE FOR REJECTION.
3. You have to enter your Roll Number on the Test Booklet in the Box provided alongside. **DO NOT** write *anything else* on the Test Booklet.
4. This Test Booklet contains **120** items (questions). Each item comprises four responses (answers). You will select the response which you want to mark on the Answer Sheet. In case you feel that there is more than one correct response, mark the response which you consider the best. In any case, choose **ONLY ONE** response for each item.
5. You have to mark your responses **ONLY** on the separate Answer Sheet provided. See directions in the Answer Sheet.
6. All items carry equal marks.
7. Before you proceed to mark in the Answer Sheet the response to various items in the Test Booklet, you have to fill in some particulars in the Answer Sheet as per instructions sent to you with your Admission Certificate.
8. After you have completed filling in all your responses on the Answer Sheet and the examination has concluded, you should hand over to the Invigilator **only the Answer Sheet**. You are permitted to take away with you the Test Booklet.
9. Sheets for rough work are appended in the Test Booklet at the end.
10. **Penalty for wrong answers :**  
**THERE WILL BE PENALTY FOR WRONG ANSWERS MARKED BY A CANDIDATE.**
  - (i) There are four alternatives for the answer to every question. For each question for which a wrong answer has been given by the candidate, **one-third (0.33)** of the marks assigned to that question will be deducted as penalty.
  - (ii) If a candidate gives more than one answer, it will be treated as **wrong answer** even if one of the given answers happens to be correct and there will be same penalty as above to that question.
  - (iii) If a question is left blank i.e. no answer is given by the candidate, there will be **no penalty** for that question.

**DO NOT OPEN THIS TEST BOOKLET UNTIL YOU ARE ASKED TO DO SO**

1. The coordination number and the atomic packing factor for Hexagonal Close Packed (HCP) and Face-Centred Cubic Crystal Structure are respectively
  - (a) 8 and 0.74
  - (b) 12 and 0.68
  - (c) 8 and 0.68
  - (d) 12 and 0.74
2. The resistivity of material is a function of temperature because
  - (a) electron density varies with temperature
  - (b) electron gas density varies with temperature
  - (c) amplitude of vibration of atom varies with temperature
  - (d) All of the above
3. Medium doping in Silicon and Germanium corresponds to impurity of the order of
  - (a) 1 part in  $10^6$
  - (b) 1 part in  $10^5$
  - (c) 1 part in  $10^4$
  - (d) 1 part in  $10^8$
4. An electric field is applied to a semiconductor. Let the number of charge carrier be  $n$  and the average drift speed be  $v$ . If the temperature is increased then
  - (a) both  $n$  and  $v$  will increase
  - (b)  $n$  will increase but  $v$  will decrease
  - (c)  $v$  will increase but  $n$  will decrease
  - (d) both  $n$  and  $v$  will decrease
5. In a piezoelectric crystal oscillator, if  $x$  represents the mass of the crystal, then the oscillation or tuning frequency is linearly proportional to
  - (a) the mass of the crystal
  - (b) the square root of the mass of the crystal
  - (c) the square of the mass of the crystal
  - (d) the inverse of the square root of the mass of the crystal
6. The temperature above which an antiferromagnetic material becomes paramagnetic is called
  - (a) Neel temperature
  - (b) Peak temperature
  - (c) Critical temperature
  - (d) Weiss temperature
7. The relative permeability is less than 1 in
  - (a) ferromagnetic materials
  - (b) diamagnetic materials
  - (c) paramagnetic materials
  - (d) ferrites

8. Which one of the following quantities can be measured with the help of the piezoelectric crystal ?
- (a) Acceleration
  - (b) Flow
  - (c) Temperature
  - (d) Velocity
9. As per Curie-Weiss law, the magnetic susceptibility of a material varies as
- (a)  $T^{-2}$
  - (b)  $1/T$
  - (c)  $T$
  - (d)  $T^2$
10. Ferrites have
- (a) low copper loss
  - (b) low eddy current loss
  - (c) low resistivity
  - (d) higher specific gravity than that of the iron
11. Two lamps each of 230 V and 60 W rating are connected in series across a single phase 230 V supply. The total power consumed by the two lamps would be
- (a) 120 W
  - (b) 60 W
  - (c) 30 W
  - (d) 15 W
12. Two charges are placed at a small distance apart. If a glass slab is placed between them, the force between the charges will
- (a) not change
  - (b) increase
  - (c) decrease
  - (d) reduce to zero
13. The total capacitance of two capacitors is 25 F when connected in parallel and 4 F when connected in series. The individual capacitances of the two capacitors are
- (a) 1 F and 24 F
  - (b) 3 F and 21 F
  - (c) 5 F and 20 F
  - (d) 10 F and 15 F
14. A coil having an inductance of 4 H and a resistance of  $2 \Omega$  is connected across a 20 V dc source. The steady-state current (in amperes) through the coil is
- (a) 5
  - (b) 3.3
  - (c) 10
  - (d) 6.6
15. An electric motor is developing 10 kW at a speed of 900 rpm. The torque available at the shaft is
- (a) 106 N-m
  - (b) 66 N-m
  - (c) 1600 N-m
  - (d) 90 N-m

16. A heavily doped semiconductor has
- (a) a resistivity which decreases exponentially with temperature
  - (b) a resistivity which rises almost linearly with temperature
  - (c) a negative temperature coefficient of resistance
  - (d) a positive temperature coefficient of resistance

17. A Zener diode has the following properties :

1. It is properly doped crystal diode with sharp breakdown
2. It is reverse biased
3. Its forward characteristics are just that of ordinary diode
4. Its reverse characteristics are like ordinary diode

- (a) 1, 2, 3 and 4
- (b) 1, 2 and 4 only
- (c) 1, 2 and 3 only
- (d) 3 and 4 only

18. A tunnel diode is a  $p-n$  junction in which


- (a)  $n$ -region is degenerately doped
- (b)  $p$ -region is degenerately doped

- (c) either  $n$  or  $p$ -region is degenerately doped
- (d) both  $n$  and  $p$ -regions are degenerately doped

19. Which is the diode used for measuring light intensity ?

- (a) Junction diode
- (b) Varactor diode
- (c) Tunnel diode
- (d) Photo diode

20.

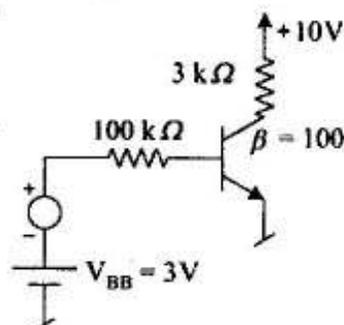


The trans-conductance  $g_m$  of the transistor used in the CE amplifier shown in the above circuit, operating at room temperature is

- (a) 92 mA/V
- (b) 46 mA/V
- (c) 184 mA/V
- (d) 25 mA/V

21. Which of the following are essentials of a transistor biasing circuit ?
1. Proper zero signal collector current flow
  2.  $V_{CE}$  should not fall below 0.5 V for Germanium and 1 V for Silicon
  3. Ensure stabilization of operating point
  4. Loading to the source
- (a) 1, 2 and 3 only  
 (b) 1, 2 and 4 only  
 (c) 3 and 4 only  
 (d) 1, 2, 3 and 4
22. When a transistor is saturated,
- (a) the emitter potential is more than the base-collector potential
  - (b) the collector potential is more than the base-emitter potential
  - (c) the base potential is more than the emitter-collector potential
  - (d) the base, emitter and collector are almost the same potential
23. If the  $\alpha$  value of a transistor changes 0.5% from its nominal value of 0.9, the percentage change in  $\beta$  will be
- (a) 0%
  - (b) 2.5%
  - (c) 5%
  - (d) 7.5%
24. If an npn silicon transistor is operated at  $V_{CE} = 5$  V and  $I_C = 100$   $\mu$ A and has a current gain of 100 in the CE connection, then the input resistance of this circuit will be
- (a) 250  $\Omega$
  - (b) 25 k $\Omega$
  - (c) 250 k $\Omega$
  - (d) 2500 k $\Omega$
25. In a bipolar junction transistor an increase in magnitude of collector voltage increases the space-charge width at the output junction diode. This causes the effective base width to decrease. This effect is known as
- (a) Hall effect
  - (b) Early effect
  - (c) Miller effect
  - (d) Zener effect
26. Which type of protection is provided for SCR by connecting the snubber circuit across it ?
- (a)  $\frac{dv}{dt}$  protection
  - (b)  $\frac{di}{dt}$  protection
  - (c) Over-voltage protection
  - (d) Over-current protection

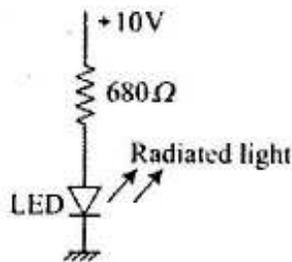27. A capacitor of  $100 \mu\text{F}$  is charged to  $10 \text{ V}$  through a resistance of  $10 \text{ k}\Omega$ . It would be fully charged in
- 5 sec
  - 0.1 sec
  - 1.0 sec
  - 0.5 sec
28. Most of the linear ICs are based on two-transistor differential amplifiers because of
- input voltage-dependent linear transfer characteristic
  - high voltage gain
  - high input resistance
  - high CMRR
29. When the photo resist coating (during IC fabrication) is exposed to ultraviolet light the photo resist becomes
- oxidized
  - ionized
  - polymerized
  - brittle
30. For a sheet with resistivity  $\rho$ , width  $w$ , length  $l$  and thickness  $y$ , the resistance per square (sheet resistance)  $R_s$  is
- $\frac{\rho}{y}$
  - $\rho y$
  - $\frac{\rho l}{y}$
  - $\frac{\rho}{ly}$
31. An optical fibre has refractive index core
- high and low refractive index cladding
  - low and high refractive index cladding
  - uniform surrounded by variable index cladding
  - variable with refractive index increases from low at the centre to high at the junction with cladding
32. The wavelength beyond which photoelectric emission cannot take place is called
- long wavelength
  - optical wavelength
  - photoelectric wavelength
  - critical wavelength
- 33.



The Light Emitting Diode (LED), shown in the above figure has a voltage drop of  $2 \text{ V}$ . The current flowing through LED is

- 11.8 mA
- 0.0147 mA
- 2.941 mA
- 0.0176 mA

34. If a continuous time signal  $x(t)$  can take on any value in the continuous interval  $(-\infty, \infty)$ , it is called

- (a) Deterministic signal
- (b) Random signal
- (c) Analog signal
- (d) Digital signal

35. The value of the integral

$$I = \int_1^2 (5t^2 + 1) \delta(t) dt \text{ is}$$

- (a) 0
- (b) 1
- (c)  $\frac{42}{3}$
- (d)  $\frac{125}{3}$

36. A continuous time system will be BIBO stable if all the Eigen values are

- (a) one
- (b) distinct and their real parts negative
- (c) negative
- (d) zero

37. The value of  $\int_{-\infty}^{\infty} \sin t \delta\left(t - \frac{\pi}{4}\right) dt$  is

- (a)  $\sqrt{2}$
- (b)  $\frac{1}{\sqrt{3}}$
- (c)  $\frac{1}{\sqrt{2}}$
- (d)  $\sqrt{3}$

38. The forced response  $y_f(n)$  of the differential equation

$$y(n) - 0.6y(n-1) = (0.4)^n, \quad n \geq 0$$

$$y(-1) = 10$$

- (a)  $9(0.6)^n$
- (b)  $-2(0.4)^n$
- (c)  $9(0.4)^n$
- (d)  $9(0.6)^n - 2(0.4)^n$

39. The ramp function can be obtained from the unit impulse at  $t = 0$  by

- (a) differentiating unit impulse function once
- (b) differentiating unit impulse function twice
- (c) integrating unit impulse function once
- (d) integrating unit impulse function twice

40. Homogeneous solution of


$$y(n) - \frac{9}{16}y(n-2) = x(n-1) \text{ is}$$

- (a)  $C_1\left(\frac{3}{4}\right)^n + C_2\left(-\frac{3}{4}\right)^n$
- (b)  $C_1\left(-\frac{3}{4}\right)^{n-1} + C_2\left(\frac{3}{4}\right)^{n-1}$
- (c)  $C_1\left(\frac{3}{4}\right)^n$
- (d)  $C_1\left(-\frac{3}{4}\right)^n$

41. A source of (power/energy) feeds the input port of an amplifier and the output port is connected to a 'load'. The input impedance of the ideal amplifier should ideally be

- (a) zero
- (b)  $\infty$
- (c) low
- (d) high

42.

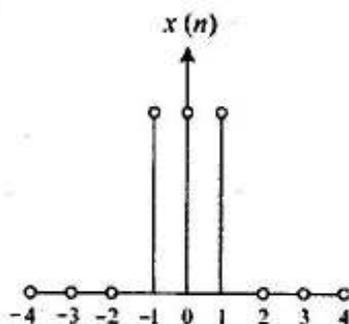

The signal  $x(n)$  shown in the above figure is a

- (a) periodic discrete time signal
- (b) periodic signal
- (c) non-periodic signal
- (d) periodic discrete time signal consisting of 3 non-zero samples

43. Which of the following Dirichlets conditions are correct for convergence of Fourier transform of the function  $x(t)$  ?

- 1.  $x(t)$  is square integrable
- 2.  $x(t)$  must be periodic
- 3.  $x(t)$  should have finite number of maxima and minima within any finite interval
- 4.  $x(t)$  should have finite number of discontinuities within any finite interval

- (a) 1, 2, 3 and 4
- (b) 1, 2 and 4 only
- (c) 1, 3 and 4 only
- (d) 2, 3 and 4 only

44. If  $f(t)$  is a real and odd function, then its Fourier transform  $F(\omega)$  will be

- (a) real and even function of  $\omega$
- (b) real and odd function of  $\omega$
- (c) imaginary and odd function of  $\omega$
- (d) imaginary function of  $\omega$

45. For certain sequences which are neither absolutely summable nor square summable, it is possible to have a Fourier Transform (FT) representation if we

- (a) take short time FT
- (b) evaluate FT only the real part of the sequence
- (c) allow DTFT to contain impulses
- (d) evaluate FT over a limited time span

46. A unit impulse function  $\delta(t)$  is defined by

1.  $\delta(t) = 0$  for all  $t$  except  $t = 0$

2.  $\int_{-\infty}^{\infty} \delta(t) dt = 1$

The Fourier transform  $F(\omega)$  of  $\delta(t)$  is

- (a) 1
- (b)  $\frac{1}{\omega}$
- (c) 0
- (d)  $\frac{1}{j\omega}$

47. The convolution  $x(n) * \delta(n - n_0)$  is equal to

- (a)  $x(n - n_0)$
- (b)  $x(n + n_0)$
- (c)  $x(n_0)$
- (d)  $x(n)$

48. If the  $z$ -transform of

$$x(n) \text{ is } x(z) = \frac{z(8z-7)}{4z^2-7z+3}, \text{ then the}$$

$\lim_{n \rightarrow \infty} x(n)$  is

- (a) 1
- (b) 2
- (c)  $\infty$
- (d) 0

49. The final value theorem is

- (a)  $\lim_{k \rightarrow \infty} x(k) = \lim_{z \rightarrow 1} (z-1)X^+(z)$
- (b)  $\lim_{k \rightarrow \infty} x(k) = \lim_{z \rightarrow 1} X^+(z)$
- (c)  $\lim_{k \rightarrow \infty} x(k) = \lim_{z \rightarrow 0} (z^{-1})X^+(z)$
- (d)  $\lim_{k \rightarrow \infty} x(k) = \lim_{z \rightarrow 0} (z-1)^{-1}X^+(z^{-1})$

50. For the discrete signal  $x[n] = a^n u[n]$  the  $z$ -transform is

- (a)  $\frac{z}{z+a}$
- (b)  $\frac{z-a}{z}$
- (c)  $\frac{z}{a}$
- (d)  $\frac{z}{z-a}$

51. If the power spectral density is  $\frac{\eta}{2} \frac{W}{Hz}$ , and the auto correlation function is defined by

$$R(\tau) = \frac{\eta}{2} \int_{-\infty}^{\infty} e^{j\omega\tau} df$$


The integral on the right represents the Fourier transform of

- (a) Delta function
- (b) Step function
- (c) Ramp function
- (d) Sinusoidal function

52. A battery is connected to a resistance causing a current of 0.5 A in the circuit. The current drops to 0.4 A when an additional resistance of 5  $\Omega$  is connected in series. The current will drop to 0.2 A when the resistance is further increased by

- (a) 10  $\Omega$
- (b) 15  $\Omega$
- (c) 25  $\Omega$
- (d) 40  $\Omega$


53.

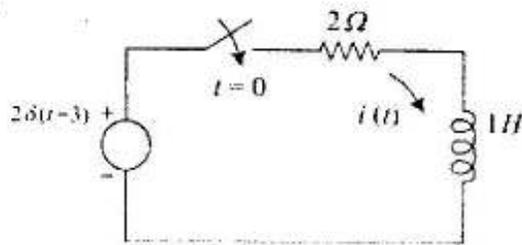

For the network shown above, the current  $i(t)$  is

- (a)  $2e^{-2(t-3)} u(t-3)$
- (b)  $0.5e^{-2(t-3)} u(t)$
- (c)  $2e^{-(t-3)} u(t-3)$
- (d)  $2e^{-(t-3)} u(t)$

54.

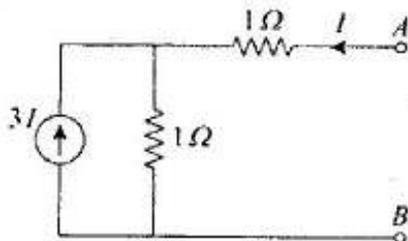


In the circuit shown above, the Thevenin resistance seen from the terminals  $AB$  is

- (a)  $1 \Omega$
- (b)  $1.5 \Omega$
- (c)  $3 \Omega$
- (d)  $5 \Omega$

55. A network  $N$  consists of resistors and independent voltage and current sources. Its value of the determinant based on the node analysis

- 1. cannot be negative
  - 2. cannot be zero
  - 3. is independent of the values of voltages and current sources
- (a) 1, 2 and 3
  - (b) 1 and 2 only
  - (c) 2 and 3 only
  - (d) 1 and 3 only

56.

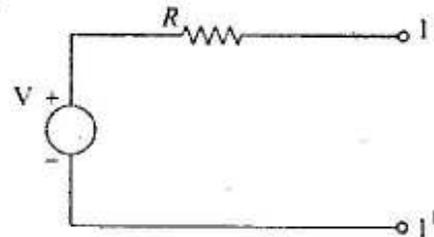

Thevenin equivalent circuit of a network  $N$  is shown above (at terminals  $1 - 1'$ ).

To determine the value of  $R$

- 1. all initial conditions are set to zero
  - 2. all independent sources are turned off
  - 3. all controlled sources are turned off
  - 4. small load connected to terminals  $1 - 1'$  (outside network  $N$ ) is removed
- (a) 1 and 2 only
  - (b) 1, 2 and 4
  - (c) 3 and 4 only
  - (d) 3 only

57. Consider the following data :


1. Input applied for  $t < t_0$
2. Input applied for  $t \geq t_0$
3. State of the network at  $t = t_0$
4. State of the network at  $t < t_0$

Which of these are needed for determining the response of a linear network for  $t < t_0$  ?

- (a) 1, 3 and 4
  - (b) 2, 3 and 4
  - (c) 2 and 3 only
  - (d) 2 and 4 only
58. If a capacitor is energized by a symmetrical square wave current source, then the steady-state voltage across the capacitor will be a

- (a) square wave
- (b) triangular wave
- (c) step function
- (d) impulse function


59.

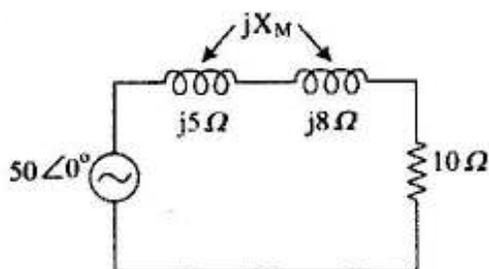

The power absorbed by the network excited by a  $50 \angle 0^\circ$  sinusoidal source is 168 W. The value of the mutual inductive reactance  $jX_M$  should be

- (a)  $13 \Omega$
- (b)  $10 \Omega$
- (c)  $6.3 \Omega$
- (d)  $3 \Omega$


60.

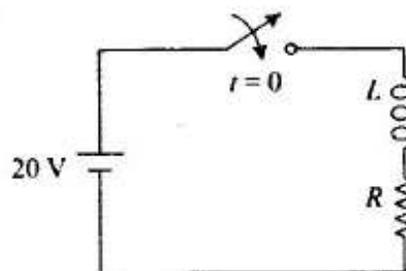

The circuit shown above ( $L = 2 H$  and  $R = 4 \Omega$ ) is switched across a D.C. power supply of 20 V. The current at time  $t = 1$  sec is

- (a) 5 A
- (b) 4.32 A
- (c) 2 A
- (d) 0.5 A

61.

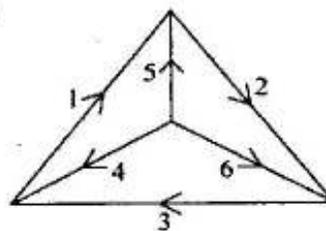

For the oriented graph as given above, taking 4, 5, 6 as tree branches the tie set matrix is

- (a) 
$$\begin{bmatrix} -1 & 0 & 0 & -1 & 1 & 0 \\ 0 & -1 & 0 & 0 & -1 & 1 \\ 0 & 0 & -1 & 1 & 0 & -1 \end{bmatrix}$$
- (b) 
$$\begin{bmatrix} 1 & 0 & 0 & 1 & -1 & 0 \\ 0 & 1 & 0 & 0 & 1 & -1 \\ 0 & 0 & 1 & -1 & 0 & 1 \end{bmatrix}$$
- (c) 
$$\begin{bmatrix} 1 & -1 & 0 & -1 & 1 & 0 \\ 1 & 0 & 0 & 0 & -1 & 1 \\ 0 & 0 & 1 & 1 & 0 & -1 \end{bmatrix}$$
- (d) 
$$\begin{bmatrix} -1 & 0 & 0 & -1 & 0 & 0 \\ 0 & -1 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 & -1 \end{bmatrix}$$


62. The number of branches in a network is  $b$ , the number of nodes is  $n$  and number of dependent loop is  $l$ . The number of independent current equations will be

- (a)  $n - l - 1$
- (b)  $b - l$
- (c)  $b - n$
- (d)  $n - 1$

63. Two two-port networks are connected in cascade. The combination is to be represented as a single two-port network. The parameters are obtained by multiplying the individual

- (a)  $h$ -parameter matrix
- (b)  $ABCD$  parameter matrix
- (c)  $Y$ -parameter matrix
- (d)  $Z$ -parameter matrix


64.

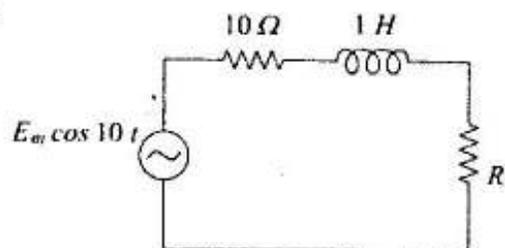

In the above circuit, the value of the load resistance  $R$  to absorb the maximum power is

- (a)  $14.14 \Omega$
- (b)  $10 \Omega$
- (c)  $200 \Omega$
- (d)  $28.28 \Omega$

65.

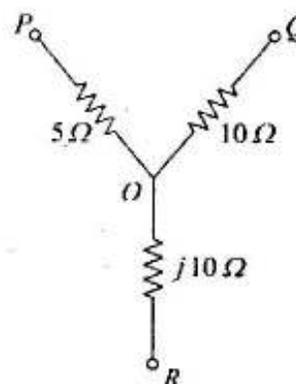

In the delta equivalent of the above star connected circuit,  $Z_{QR}$  is equal to

- (a)  $40 \Omega$
- (b)  $(20 + j10) \Omega$
- (c)  $(5 + j\frac{10}{3}) \Omega$
- (d)  $(10 + j30) \Omega$

66. In the following statements, choose the correct combination(s) :

1. If  $z_{11} = z_{22}$  and  $|h| = 1$  the network is symmetric
2. If  $h_{11} = h_{12}$  the network is symmetric
3. If  $h_{12} = -h_{21}$  the network is reciprocal
4. If  $A^2 - BC = 0$  the network is reciprocal

- (a) 1 and 3
- (b) 3 and 4
- (c) 1 and 4
- (d) 2 and 3

67. The transmission parameters in inverse hybrid (g) parameter form are expressed in terms of the

- current of input port 1 and voltage of the output port 2 and which are expressed in terms of the input voltage and output current
- input voltage and current of the input port 1 and which are expressed in terms of the output voltage and current of the output port 2
- input voltage and output currents of port 1 and port 2 respectively and which are expressed in terms of the input current and output voltage of port 1 and port 2 respectively
- None of the above


68. Two identical 2-port networks  $N_A$  and  $N_B$  are connected in cascade to form a composite network  $N$ . The transmission parameters of  $N$  are given by the matrix

$$\begin{bmatrix} 7 & 12 \\ 4 & 7 \end{bmatrix}$$

The transmission matrix for the individual network is

- $\begin{bmatrix} 3.5 & 6 \\ 2 & 3.5 \end{bmatrix}$
- $\begin{bmatrix} 14 & 24 \\ 8 & 14 \end{bmatrix}$
- $\begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix}$
- $\begin{bmatrix} 3 & 2 \\ 2 & 1 \end{bmatrix}$

69.

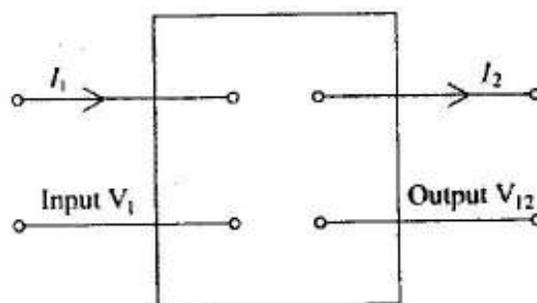

The condition of symmetry in  $ABCD$  parameters in the system shown above will be

- $A = D$
- $B = \frac{1}{A}$
- $A = \frac{1}{B}$
- $B = D$

70. Which of the following statements are **not** true for the driving point functions of a lossless network ?


- They are the ratio of odd to even or even to odd polynomials.
- They do not satisfy the separation property.
- They have either a pole or a zero at the origin and infinity.
- Their degrees of the numerator and denominator polynomials differ by 2 and only 2.

- 1 and 2
- 1 and 3
- 2 and 3
- 2 and 4

71. For a driving point function, with  $n$  = degree of numerator polynomial and  $m$  = degree of denominator polynomial, the relationship connecting  $n$  and  $m$  is

- (a)  $|n - m| \leq 1$   
 (b)  $|n - m| = 0$   
 (c)  $(n - m) < -1$   
 (d)  $n - m > 1$

72.

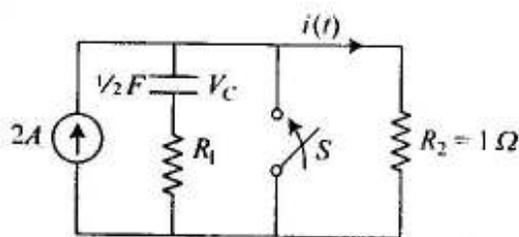


After closing the switch  $S$  at  $t = 0$ , the current  $i(t)$  at any instant  $t$  in the above network is

- (a)  $10 + 10e^{100t}$   
 (b)  $10 - 10e^{100t}$   
 (c)  $10 + 10e^{-100t}$   
 (d)  $10 - 10e^{-100t}$

73. If  $Z(s) = \frac{s^3 + 10s^2 + 25s + 18}{(s+1)(s+3)(s+5)}$ , it is

- (a) an RC driving-point impedance  
 (b) an RL driving-point impedance  
 (c) an LC driving-point impedance  
 (d) None of the above

74.

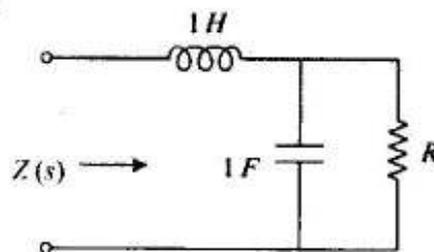

The driving-point impedance  $Z(s)$  of the circuit shown in the above figure is

- (a)  $\frac{s^2 + Rs}{1 + Rs}$   
 (b)  $\frac{Rs^2 + s + R}{Rs + 1}$   
 (c)  $\frac{s^2(R+1) + 3}{1 + Rs}$   
 (d)  $\frac{1}{(1 + Rs)^2}$

75. Which of the following are electromagnetic in nature ?

1. Alpha rays
2. X-rays
3. Gamma rays
4. Cathode rays

- (a) 1 and 2  
 (b) 2 and 3  
 (c) 3 and 4  
 (d) 1 and 4

76. The ratio of the charges stored by two metallic spheres raised to the same potential is 6. The ratio of the surface area of the sphere is

- (a) 6
- (b)  $\frac{1}{6}$
- (c) 36
- (d)  $\frac{1}{\sqrt{6}}$

77. The field strength of a plane wave is 2 V/m. The strength of the magnetic field (H) in free space is

- (a) 5.2 mA/m
- (b) 2.25 mA/m
- (c) 250 mA/m
- (d) 520 mA/m

78. A coil of inductance 2 H and resistance 1  $\Omega$  is connected to a 10 V battery with negligible internal resistance. The amount of energy stored in the magnetic field is

- (a) 8 J
- (b) 50 J
- (c) 25 J
- (d) 100 J

79. Electric displacement current density  $D$  at any point on a spherical surface of radius  $r$  centred at the isolated charge  $q$  is

- (a)  $\frac{q^2}{r^2}$
- (b)  $\frac{q}{r^2}$
- (c)  $\frac{q}{4\pi r^2}$
- (d)  $\frac{q}{4\pi^2 r^2}$

80. Consider a uniform sphere of charge density  $\rho_0$  and radius  $b$  centred at the origin. The electric field at a radial distance  $r$  ( $r < b$ ), according to Gauss's law, is

- (a)  $\frac{\gamma\rho_0}{3\epsilon}$
- (b)  $\frac{\rho_0}{4\pi\epsilon r^2}$
- (c)  $\frac{b^3\rho_0}{3\epsilon r^2}$
- (d)  $\frac{\rho_0}{\gamma}$

where  $\epsilon$  is the permittivity.

81. At a point  $(x, y, z)$  potential is given by  $A(x^2 + y^2 + z^2)$ . The potential difference between points  $P(1, 0, 2)$  and  $Q(1, 1, 2)$  is

- (a) 8 V
- (b) 8 A V
- (c) 9 A V
- (d) 9 V

82. The intrinsic impedance  $\eta$  of a conducting medium for which  $\sigma = 58 \text{ Ms/m}$ ,  $\mu_r = 1$  at a frequency of 100 MHz is

- (a)  $2.14 \times 10^5 \angle 45^\circ \Omega$
- (b)  $1.84 \times 10^{-3} \angle 45^\circ \Omega$
- (c)  $3.69 \times 10^{-3} \angle 45^\circ \Omega$
- (d)  $3.69 \times 10^{-3} \angle -45^\circ \Omega$

83. A conducting plane at  $z = 0$  has a voltage of 100 V on it.  $V_1$  and  $V_2$  are two solutions, with  $V_1 = 5z + 100$  and  $V_2 = 100$ ; which satisfy Laplace equation as well as the boundary condition  $V = 100$  at  $z = 0$ . Which of the following is the most correct option ?

- (a) Both  $V_1$  and  $V_2$  are correct and solution is not unique
- (b) Unique solution cannot be found
- (c) Only  $V_1$  is the correct solution
- (d) The given plane does not serve as a proper boundary as the reference is not given

84. If  $E = E_m \sin(\omega t - \beta_2 z) \bar{a}_y$  is free space, then  $B$  is given by

- (a)  $\frac{-E_m \beta}{\omega} \sin(\omega t - \beta_2 z) \bar{a}_z$
- (b)  $\frac{-E_m \beta}{\omega} \cos(\omega t - \beta_2 z) \bar{a}_x$

(c)  $\frac{E_m \beta}{\omega} \sin(\omega t - \beta_2 z) \bar{a}_y$

(d)  $\frac{E_m \beta}{\omega} \cos(\omega t - \beta_2 z) \bar{a}_y$

85. A uniform plane wave with an intensity of electric field 1 V/m is travelling in free space. The magnitude of associated magnetic field is

- (a) 2.65 mA/m
- (b) 2.65 A/m
- (c) 2.65  $\mu\text{A/m}$
- (d) 26.5 A/m

86. A reflectometer consists of

- (a) two directional couplers
- (b) one directional coupler and an isolator
- (c) one directional coupler and a circulator
- (d) two directional couplers and a circulator

87. A transmission line, has a characteristic impedance ( $Z_0$ ) of 600  $\Omega$ . Its length is 500 m. If the line is cut into half what will be the  $Z_0$  for each half ?

- (a)  $\frac{Z_0}{4}$
- (b)  $\frac{Z_0}{2}$
- (c)  $Z_0$
- (d)  $2Z_0$

- 88.** A plain wave is travelling in the positive X-direction in a lossless unbounded medium having permeability the same as the free space and a permittivity 9 times that of the free space, the phase velocity of the wave will be
- $3 \times 10^8$  m/s
  - $10^8$  m/s
  - $\frac{1}{3} \times 10^8$  m/s
  - $\sqrt{3} \times 10^8$  m/s
- 89.** In a semiconductor strain gauge, the change in resistance on application of strain is mainly due to change in
- length of the wire
  - diameter of the wire
  - resistivity of the material of the wire
  - both the length and diameter of the wire
- 90.** In an LVDT, the two secondary windings are connected in differential mode to obtain
- higher output voltage
  - a reduction in output impedance
  - an increase in input impedance
  - the null for particular position of core
- 91.** For an antenna, Radiation Intensity is defined as
- the time-averaged radiated power per unit solid angle
  - the peak radiated power per unit solid angle
  - the peak radiated power per unit area
  - the time-averaged radiated power per unit area
- 92.** The resistances of two coils of a watt-meter are  $0.0 \Omega$  and  $100 \Omega$  respectively and both are non-inductive. The current through a resistance load is 20 A and the voltage across it is 30 V. In one of the two ways of connecting the voltage coil, the error in the reading would be
- 0.1% too high
  - 0.2% too high
  - 0.15% too high
  - zero
- 93.** A 0-150 V voltmeter has a guaranteed accuracy of 1% full-scale reading. The voltage measured by this instrument is 83 V. The limiting error in per cent is
- 1.81%
  - 0.18%
  - 5.53%
  - 0.553%

94. The strain gauge should have

1. High gauge factor
2. Low resistance temperature coefficient
3. High resistance

Which of the above statements are correct ?

- (a) 1 and 2 only
- (b) 1 and 3 only
- (c) 2 and 3 only
- (d) 1, 2 and 3

95. The secondary of a CT is never left open-circuited because

1. The heat dissipation in the core will be very large
2. The core will be saturated and get permanently magnetized rendering it useless
3. Dangerously high emf will be induced in the secondary

Which of the above statements are correct ?

- (a) 1 and 2 only
- (b) 1 and 3 only
- (c) 1, 2 and 3
- (d) 2 and 3 only

96. A resistance strain gauge with gauge factor of 3 is subjected to a stress of 3000 kg/cm when fastened to a steel rod. The modulus of elasticity of steel is  $2.1 \times 10^6$  kg/cm<sup>2</sup>. The percentage change in resistance of the strain gauge element is

- (a) 0.1428%
- (b) 24.84%
- (c) 0.4284%
- (d) 4.3%

97. Two 100 V F.S.D. PMMC type dc voltmeters having figure of merit of 10 k $\Omega$ /V and 20 k $\Omega$ /V are connected in series. The series combination can be used to measure a maximum dc voltage of

- (a) 200 V
- (b) 175 V
- (c) 150 V
- (d) 125 V

98. The true rms responding voltmeter senses

- (a) the rms value divided by the average value of voltage
- (b) the square of the rms value of voltage
- (c) the actual rms value of voltage
- (d) the rms value divided by the peak value of voltage

99. A  $4\frac{1}{2}$  digit voltmeter is used for measurements. It would display the voltage value 0.3861 on a 10 V range as
- 0.3861
  - 0.386
  - 0.38
  - 0.38610
100. What is the dynamic range of a spectrum analyzer with a third order intercept point of +25 dBm, and a noise level of (-) 85 dBm.
- 0.73 dB
  - 7.3 dB
  - 73 dB
  - 730 dB
101. The bandwidth of a digitally recorded signal primarily depends upon
- the physical properties of the system components processing the signal
  - the frequency at which the signal is sampled
  - the frequency of the clock signal that is used to encode binary values responding the signal
  - the frequency of the noise affecting signal quality
102. A 10-bit A/D converter is used to digitize an analog signal in the 0-5 V range. The maximum peak-to-peak ripple voltage that can be allowed in the dc supply voltage is nearly
- 100 mV
  - 50 mV
  - 25 mV
  - 5 mV
103. The wire in a metallic strain gauge is 0.1 m long and has an initial resistance of 120 ohm. On application of an external force, the wire length increases by 0.1 mm and the resistance increases by 0.21 ohm. The gauge factor of the strain gauge will be
- 3.00
  - 2.00
  - 1.75
  - 2.85
104. An LVDT has the following specifications :
- Input = 6.3 V,  
Output = 5.2 V,  
range  $\pm 1.25$  cm.
- Then the output voltages produced due to core movement from +1.1 cm to -0.4 cm will be respectively
- +4.576 V and -1.664 V
  - +2.288 V and -0.832 V
  - +4.0 V and -1.0 V
  - +2.0 V and -1.0 V
105. A temperature sensitive transducer is subjected to a sudden temperature change. It takes 10 sec for the transducer to reach steady-state. The time taken by the transducer to read half of the temperature difference will be nearly
- 1.38 sec
  - 5.00 sec
  - 8.62 sec
  - 10 sec

**106.** A 1 m length wire has a resistance of  $150 \Omega$ . When it is subjected to strain, its length becomes 1.01 m. The measurement is conducted by a strain gauge whose gauge factor is 2. The change in resistance of the wire is

- (a)  $0.5 \Omega$
- (b)  $1.0 \Omega$
- (c)  $2.0 \Omega$
- (d)  $3.0 \Omega$

**107.** While measuring the voltage developed by a thermocouple, it is found that there is always an offset voltage. This is due to

- (a) a voltage across a thermocouple even at very low temperature
- (b) some photoelectric voltage across the junction due to ambient light
- (c) a barrier potential across the junction
- (d) an additional thermocouple is formed due to the connecting wires and one of the metals

**108.** An LVDT (linear variable differential transformer) produces an output of 24 V rms for a displacement of  $25 \times 10^{-3}$  cm. This voltage is measured with a 5 V full-scale voltmeter with 100 major divisions, each major division readable to 0.2 divisions. The resolution of the voltmeter is

- (a) 0.125 mm
- (b) 31.25 mm
- (c) 1.25 mm
- (d) 3.125 mm

**Directions :**

Each of the next Twelve (12) items consists of two statements, one labelled as the 'Statement (I)' and the other as 'Statement (II)'. You are to examine these two statements carefully and select the answers to these items using the codes given below :

Codes :

- (a) Both Statement (I) and Statement (II) are individually true and Statement (II) is the correct explanation of Statement (I)
- (b) Both Statement (I) and Statement (II) are individually true but Statement (II) is *NOT* the correct explanation of Statement (I)
- (c) Statement (I) is true but Statement (II) is false
- (d) Statement (I) is false but Statement (II) is true

**109.** Statement (I) : Centre tap transformer is essential for a centre-tapped rectifier.

Statement (II) : In half wave rectification minimum two diodes are required.

**110.** Statement (I) : Power factor is a measure of the power flow in the insulator and should be low.

Statement (II) : It varies with the temperature and usually increases with the rise in temperature of the insulation.

**111.** Statement (I) : An SCR has a current-controlled negative resistance characteristic.

Statement (II) : For a given current the voltage can be determined while for a given voltage current cannot be determined.

**112. Statement (I) :** JFET is operated in depletion mode only.

**Statement (II) :** The input resistance of a MOSFET is several orders of magnitude greater than that of a JFET.

**113. Statement (I) :** Zero state response is usually referred as particular solution of the filter.

**Statement (II) :** Particular solution depends on only the input but not on the initial conditions.

**114. Statement (I) :** Zero input response is the natural response with zero initial conditions.

**Statement (II) :** Zero state response is the response with given input with zero initial conditions.

**115. Statement (I) :** Aliasing occurs when the sampling frequency is less than twice the maximum frequency in the signal.

**Statement (II) :** Aliasing is a reversible process.

**116. Statement (I) :** Sampling in one domain makes the signal to be periodic in the other domain.

**Statement (II) :** Multiplication in one domain is the convolution in the other domain.

**117. Statement (I) :** In an experiment having systematic error, increasing the sample size improves precision.

**Statement (II) :** Removing the systematic error improves accuracy.

**118. Statement (I) :** During measurement ammeter is connected in series as it has low resistance and small voltage drop.

**Statement (II) :** During measurement voltmeter is connected in parallel as it has high resistance and draws small current from the circuit.

**119. Statement (I) :** An instrumentation amplifier must have well-matched components.










**Statement (II) :** To be able to faithfully amplify differential signals, an instrumentation amplifier needs excellent common mode rejection ratio.

**120. Statement (I) :** A photodiode is an example of a photoconductive sensor.

**Statement (II) :** A photodiode can be used as either a photoconductive or a photoresistive sensor.

# UPSCPORTAL PUBLICATIONS

## Civil Services Exam (*Mains*)

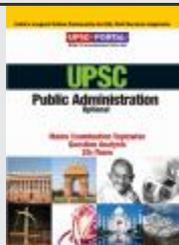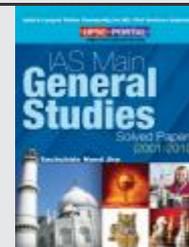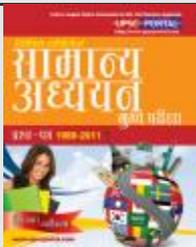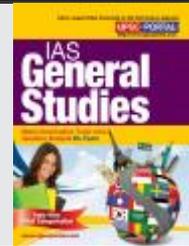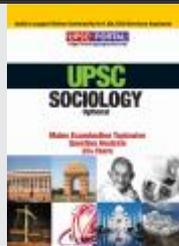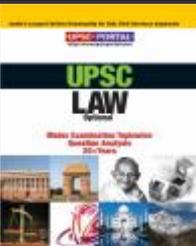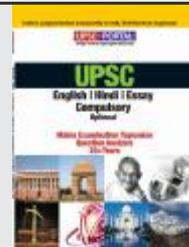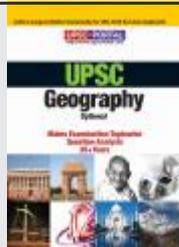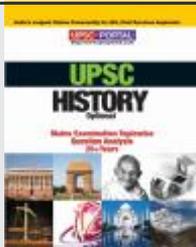


Also available at: <http://www.flipkart.com>

Helpline No. 011-45151781

Buy Online at: <http://upscportal.com/civilservices/books>

# UPSCPORTAL PUBLICATIONS

## Civil Services Exam (*Preliminary*)

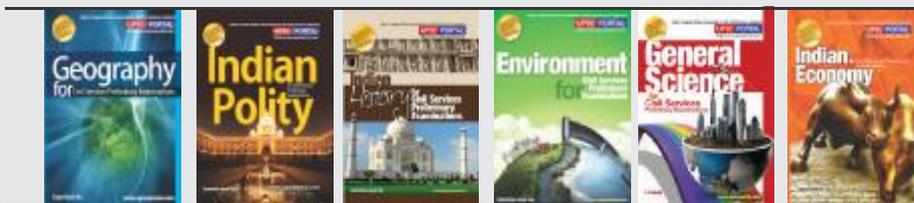












Also available at: <http://www.flipkart.com>

Helpline No. 011-45151781

Buy Online at: <http://upscportal.com/civilservices/books>

# UPSCPORTAL PUBLICATIONS

## MCQ'S SERIES

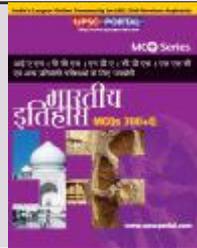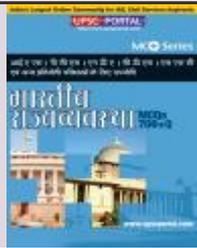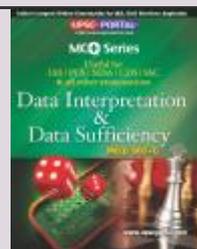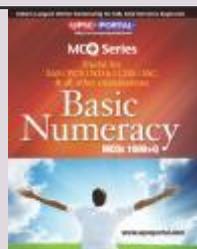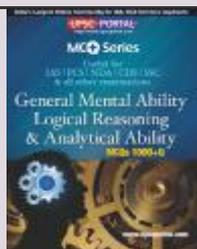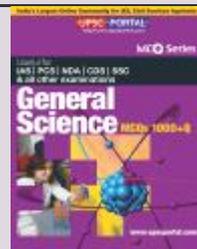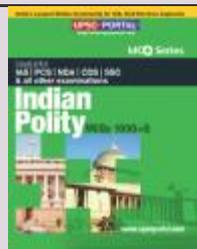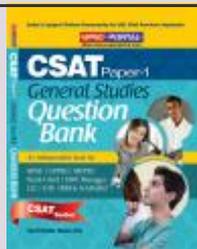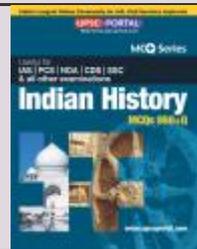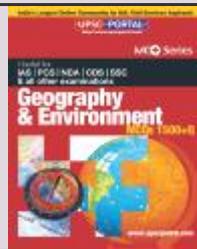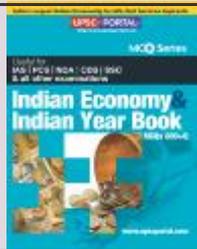

Also available at: <http://www.flipkart.com>

Helpline No. 011-45151781

Buy Online at: <http://upscportal.com/civilservices/books>

# UPSCPORTAL Study Kits for IAS, Civil Services & Other Exams

## **Study Kit for Preliminary Examinations:**

- **IAS (Pre) GS Paper 1**  
<http://upscportal.com/civilservices/study-kit/ias-pre/csat-paper-1>
- **IAS (Pre) GS Paper 2**  
<http://upscportal.com/civilservices/study-kit/ias-pre/csat-paper-2>
- **GS Foundation Course (PT+ MAINS) for 2014**  
<http://upscportal.com/civilservices/study-kit/ias-pre/general-studies-foundation-course>

## **Study Kit for Mains Examinations:**

- **Contemporary Issues**  
<http://www.upscportal.com/civilservices/study-kit/contemporary-issues-ias-mains>
- **Public Administration**  
<http://www.upscportal.com/civilservices/study-kit/ias-mains-public-adminstration>
- **Essay Writing**  
<http://www.upscportal.com/civilservices/study-kit/essay-mains>
- **English Grammar & Comprehension**  
<http://www.upscportal.com/civilservices/study-kit/ias-mains-english-compulsory>
- **History**  
<http://www.upscportal.com/civilservices/study-kit/ias-mains-history>
- **Philosophy**  
<http://upscportal.com/civilservices/study-kit/ias-mains-philosophy>
- **Sociology**  
<http://upscportal.com/civilservices/study-kit/ias-mains-sociology>
- **General Studies**  
<http://www.upscportal.com/civilservices/study-kit/gs-mains>

## **Study Kit for UPSC Other Examinations:**

- **Indian Police Service Limited Competitive Examination**  
<http://www.upscportal.com/civilservices/study-kit/ips-lce>
- **Armed Police Forces (CAPF)**  
<http://upscportal.com/civilservices/study-kit/capf>

## **Study Kit for Other Examinations:**

- **SSC Combined Graduate Level (Tier - I)**  
<http://sscportal.in/community/study-kit/cgl>
- **SSC Combined Graduate Level Examination (Tier - II)**  
<http://sscportal.in/community/study-kit/cgl-tier-2>
- **SSC Combined Higher Secondary Level (10+2) Examination**  
<http://sscportal.in/community/study-kit/chsle>



# UPSCPORTAL Online Courses

For Civil Services Preliminary & Mains Examinations

For Any Guidance Call our Expert at 011- 65023618

## Online Course for Civil Services Preliminary Examination

- ✓ Online Coaching for CSAT Paper - 1 (GS) 2014  
<http://upscportal.com/civilservices/courses/ias-pre/csat-paper-1>
- ✓ Online Coaching for CSAT Paper - 2 (CSAT) 2014  
<http://www.upscportal.com/civilservices/courses/ias-pre/csat-paper-2>
- ✓ Integrated Guidance Programme for IAS PRE (CSAT)  
<http://www.upscportal.com/civilservices/online-course/integrated-free-guidance-programme>

## Online Course for Civil Services Mains Examination

- ✓ General Studies Mains (NEW PATTERN - Paper 2,3,4,5)  
<http://www.upscportal.com/civilservices/courses/ias-mains-gs>
- ✓ Contemporary Issues for Civil Services Main Examination  
<http://www.upscportal.com/civilservices/courses/contemporary-issues>
- ✓ Public Administration for Mains  
<http://www.upscportal.com/civilservices/courses/ias-mains-pub-ad>
- ✓ Essay Programme for Mains  
<http://www.upscportal.com/civilservices/courses/ias-mains-essay>
- ✓ Free Online IAS Coaching for English Comprehension & Precis  
<http://www.upscportal.com/civilservices/courses/ias-mains-english>

## Online Course for State PSC Examination

- ✓ Madhya Pradesh Public Service Commission  
<http://upscportal.com/civilservices/courses/mppsc>

## Online Course for Other Examination

- ✓ IBPS Clerk Exam  
<http://www.bankpoclerk.com/community/online-coaching/ibps-clerk>

**B.No. A 31-34, Flat No. 201-202, Jaina Extension, 2nd Floor,  
Commercial Complex, Mukherjee Nagar, Delhi- 110009**

**PURCHASEORDERFORM**

Name: .....

Correspondance Address: .....

Email: ..... PIN CODE: .....

Phone No.: ..... City: ..... State: ..... Date: .....

S.NO.	NAME OF THE BOOKS	Pages	ISBN	PRICE
1	A01-ENGLISH LANGUAGE COMPREHENSION SKILL		9789382732006	195
2	A02-Data Interpretation		9788192051765	225
3	A03-Basic Numeracy		9789381362013	240
4	A04-Logical Reasoning & Analytical Ability.		9788192051796	230
5	A05-General Knowledge Manual ( 2013)		9789381362600	180
6	A06-English Grammer & Usage(2012)		9789381362006	220
7	A11-UPSC Pre General Science		9789381362327	250
8	A12-UPSC Pre Indian History		9789381362297	395
9	A13-UPSC Pre Environment		9789381362341	250
10	A14-UPSC Pre Indian Polity		9789381362310	350
11	A15-UPSC Pre Geography		9789381362303	315
12	A16-UPSC Pre Economy		9789382732105	260
15	A20-SAMANAY GAYAN 2013 (Hindi)		9789381362631	70
16	A21-SAMANAY GAYAN DIGDARSHIKA		9789381362617	265
17	A22-THE VALT OF ESSAY		9789381362648	340
18	A23-CONCISE GENERAL KNOWLEDGE		9789381362624	75
19	A25-CURRENT AFFAIRS 2013		9789382732358	410
20	A26-INDIA 2013		9789382732365	195
21	A27-ECONOMY SURVEY GOVERNMENT POLICIES		9789382732372	205
22	B01-CSAT PAPER-1 GENERAL STUDIES QUESTION BANK		9789382732266	185
22	B03-CSAT COMPREHENSIVE MANUAL IAS PRELIMINARY EXAMINATION PAPER-2		9789382732624	775
23	B04-UPSC PRE:G.S.Solved Q.Paper(1998-2012)		9789382732112	250
24	B05-UPSC PRE:SAMANYA ADHYAN PRARAMBHIKA PARIKSHA(2001-2012)		9789382732129	190
25	B06-2013 CSAT GENERAL STUDIES MANUAL IAS PRELIMINARY EXAMINATION PAPER -1		9789382732617	1275
26	B07-GS PRE QUESTIONS (2006-2012)		9789381362891	130
27	C01-UPSC MAINS:G.S.Papers(2013)		9789381362365	150
28	C02-UPSC MAINS:G.S. Papers HINDI(2013)		9789381362358	220
29	C03-UPSC Mains:- Geography Questions Papers		9789382732440	155
30	C04-UPSC Mains:- Sociology Questions Papers		9789382732433	120
31	C05-UPSC MAINS:ENG.Hindi Essay Questions Papers		9789382732464	155
32	C06-UPSC MAINS:- LAW Questions Papers		9789382732426	150

33	C07-UPSC MAINS: Public Ad. Questions Papers		9789382732457	155
34	C09-UPSC MAINS:- History Papers		9789382732136	155
357	C11-UPSC MAINS:G.S. Solved Paper		9789382732679	290
36	C12-UPSC MAINS:Hindi Literature Paper		9789381362525	140
37	C13-IAS MAINS HISTORY SOLVED PAPER2002-2012		9789382732686	275
38	C14-THE VAULT OF 1,2,3 & 5 MARKER (PART 1)		9789381362808	295
39	C15-THE VAULT OF 1,2,3 & 5 MARKER (PART- II)		9789381362815	225
40	D02-SSC CGL GUIDE 2012		9789381362051	360
41	D03-A COMPLETE GUIDE FOR SSC 10+2 LEVEL EXAMINATION		9789381362679	340
42	D04-SSC PRACTICE PAPERS		9789382732075	175
43	D05-SSC SOLVED PAPERS		9789382732082	175
44	D06- SUCCESS BOOK SERIES GEOGRAPHY		9789382732181	80
45	D07- SUCCESS BOOK SERIES HISTORY		9789382732174	80
46	D08-SUCCESS BOOK SERIES INDIAN POLITY		9789382732228	75
47	D09-SUCCESS BOOK SERIES GENERAL SCIENCE		9789382732198	80
48	D10-SUCCESS BOOK SERIES GENERAL KNOWLEDGE		9789382732204	75
49	D11-SUCCESS BOOK SERIES INDIAN ECONOMY		9789382732211	80
50	D12-SUCCESS BOOK SERIES BHARTIYA RAJYAVASTHA		9789382732303	80
51	D13-SUCCESS BOOK SERIES BHARTIYA ITIHAS		9789382732297	85
52	D14-SUCCESS BOOK SERIES BHUGOL PARYAVARAN		9789382732310	70
53	D15-An Authentic Book for SSC Tier - 2 Examination		9789382732600	250
54	E03-SBI. Guide		9789381362105	210
55	E04-IBPS Guide for Clerk Grade		9789381362266	280
56	E05-A COMPLETE GUIDE FOR SBI AND ASSOCIATE BANK CLERK EXAMINATION		9789381362655	295
57	E06-BHARTIYA STATE BANK CLERK BHARTI PARIKSHA		9789381362662	290
58	E07-IBPS WORK BOOK FOR CLERK EXAMINATION		9789381362884	90
59	E08-SBI BANK PO EXAMINATION PRACTICE SET PAPERS		9789382732235	265
60	E09-I.B.P.S. P.O. Guide (Hindi)		9789382732488	265
61	E10-I.B.P.S. Practice Papers (English)		9789382732495	170
62	E11-I.B.P.S. Practice Papers (Hindi)		9789382732501	165
63	E12—I.B.P.S. Solved papers (English)		9789382732518	170
64	E13-I.B.P.S. Solved papers (Hindi)		9789382732525	165
65	E14-I.B.P.S. P.O GUIDE (ENGLISH)		9789382732471	365
66	F01-CDS Solved Paper		9789381362129	295
67	F02-NDA NA Solved Paper		9789381362136	325
68	F03-SCRA-Practice Book Solved Papers		9789381362280	325
69	F04-A COMPREHENSIVE GUIDE FOR CAPF		9789381362785	310
70	F05-NDA PRACTICE PAPERS		9789382732013	200
71	F06-SCRA PRACTICE PAPERS		9789382732051	220
72	F07-CDS PRACTICE PAPERS		9789382732037	200
73	F08-LIC AAO		9789382732341	390
74	F09-DSSSB(HINDI)		9789382732273	290
75	F10-DSSSB(ENGLISH)		9789382732280	320
76	F11-A Authentic Practice Book for Delhi Police S.I. & CAPFs S.I.   CISF (A.S.I) Examination		9789382732396	170
77	F12- A Authentic Guide for Delhi Police S.I. & CAPFs S.I.   CISF (A.S.I) Examination		9789382732389	375
78	F13-GIC Assistants in Public Sector: General Insurance Companies		9789382732594	380
79	F14-UTTER PRADESH LEKHPAL BHARTI PRARIKSHA		9789382732693	150
80	F15-utter pradesh arakshi bharti parikasha 2013		9789382732662	155

81	G01-Geography & Environment MCQ		9789381362402	160
82	G02-General Science MCQ		9789381362433	120
83	G03-Indian Polity MCQ		9789382732259	95
84	G04-Indian History MCQ		9789382732327	95
85	G05-Basic Numeracy MCQ		9789381362464	130
86	G06-Indian Economy & Year Book MCQ		9789381362440	120
87	G07-Reasoning Analytical Ability MCQ		9789381362488	130
88	G08-DIDS MCQ		9789381362471	130
89	G09-Bhartiya Itihas		9789381362587	95
90	G10-Bhartiya Rajyavyavastha		9789381362570	80
91	G11-SSC MCQ		9789381362686	80

<b>Total Unit</b>	
-------------------	--

- All dispute will be settled in Delhi Jurisdiction.

DD. No.: ..... Amount (in words): .....  
Date: ..... Name of Bank & City: .....

(Sign)
--------